

Student 1

- (a) *So that current can be changed.*
- (b) (i) *When voltage is increased, the current increases too. But the graph is a curve - so as voltage goes up higher, the current doesn't go up as quickly. The curve tails off.*
- (ii) $V = I \div R$
- (iii) *On the graph, when $V = 2.5$, current = 0.09*
 $V = I \div R$ so $R = V \div I$
 $= 2.5 \div 0.09$
 $R = 27.77777777 \Omega$
- (c) *It goes up and then goes down.*

Student 2

- (a) R is a resistor.
- (b) (i) When the voltage goes up the current goes up so the current is proportional to the voltage.
- (ii) $V = C \times R$
- (iii) $2.5 = 0.084 \times R$
 $R = 2.5 \div 0.084$
 $= 2.416$
- (c) Nothing happens.